

Name: FALL 2017 SOLUTIONS

Read each question carefully before answering. Answer all parts. Show all work, calculations, and/or reasoning, otherwise no points will be awarded. Properly labeled loops must be shown on K-maps. Point values are as indicated.


1. (10 points) Implement the following minterm expression with a 4 to 1 MUX and a minimum number of external gates. Include the MUX equation and properly label the circuit diagram.

$$F(A, B, C, D) = \sum m(0, 2, 7, 8, 10, 13, 14) + \sum d(3, 9, 12)$$

	AB			
CD	00	01	11	10
00	1	0	X	1
01	0	0	1	X
11	X	1	0	0
10	1	0	1	1


Handwritten annotations on the K-map:

 - Group 1 (minterms 0, 2, 8, 10): $A'D'(B')$
- Group 2 (minterms 0, 4, 8, 12): $A'D(C)$
- Group 3 (minterms 1, 3, 5, 7): AD'
- Group 4 (minterms 13, 15): $AD(C')$




$$F = A'D'(B') + A'D(C) + AD'(1) + AD(C')$$

 2. (10 points) Fill out the following timing diagram for the output F of the given 4 to 1 MUX. Ignore all gate delays.




3. (10 points) Design a 3 to 1 MUX using only 2 to 1 multiplexers. Include a truth table and a circuit diagram of your multiplexer design.


A	B	Z
0	0	I_0
0	1	I_1
1	0	I_2
1	1	X

 

-OR-

 

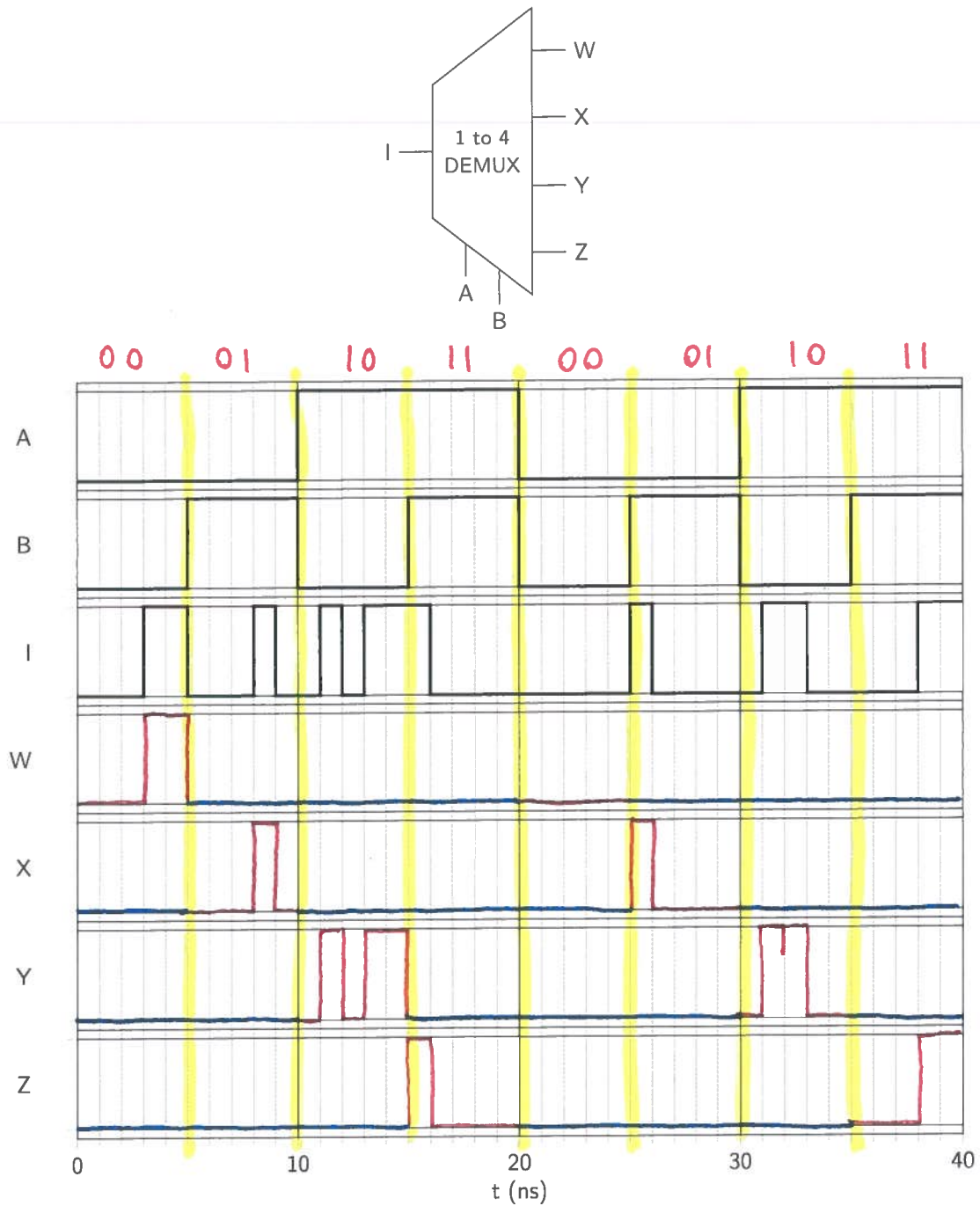
4. (10 points) Fill out the following timing diagram for the outputs W, X, Y, and Z of the given 1 to 4 DEMUX. Ignore all gate delays.



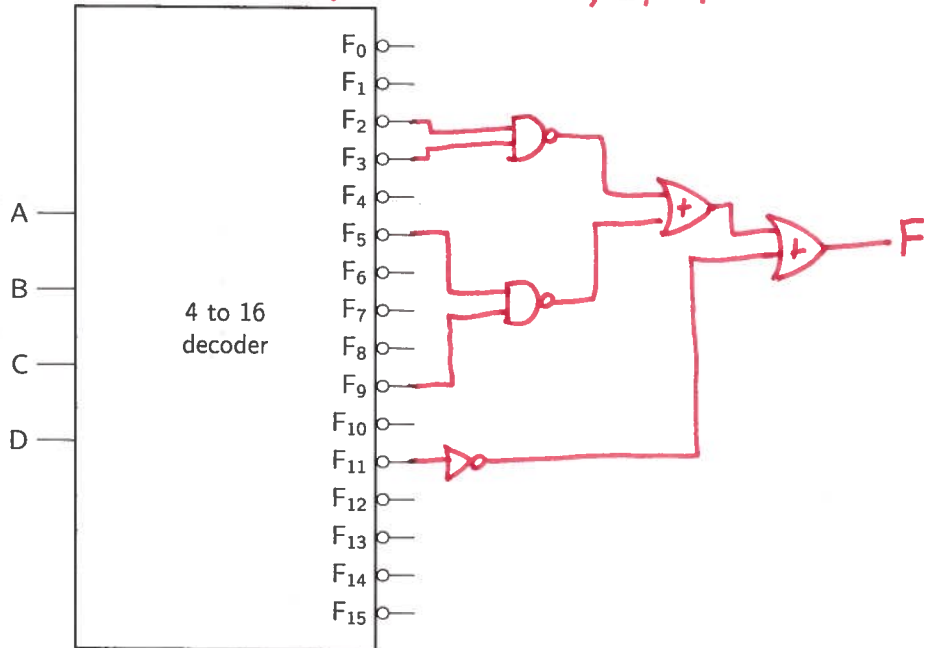
5. (10 points) Use the outputs from the following 4 to 16 decoder and a minimum number of **2-input** external gates to realize the following Maxterm expression. Properly label the circuit diagram.

oops!

$$F(A, B, C, D) = \prod M(0, 4, 6, 10, 13, 14, 15) + \prod D(1, 7, 8, 12)$$
$$= \sum m(2, 3, 5, 9, 11) + \sum d(1, 7, 8, 12)$$




 6. (10 points) Fill out the following timing diagram for an SR latch. Ignore all gate delays. $Q(0) = 1$.



0-6 ns
HOLD
6-9 ns
RESET
9-11 ns
HOLD
11-12 ns
SET
12-13 ns
HOLD
13-14 ns
RESET

 7. (10 points) Fill out the following timing diagram for an active-low gated D latch. Ignore all gate delays. $Q(0) = 0$.




14-19 ns
HOLD
19-27 ns
SET
27-28 ns
HOLD
28-30 ns
RESET
30-31 ns
HOLD
31-40 ns
SET

NOT ENABLED: 3-7 ns, 11-16 ns, 21-26 ns,
31-34 ns, 38-40 ns


SET: WHEN $\overline{EN} = 0$ AND $D = 1$

RESET: WHEN $\overline{EN} = 0$ AND $D = 0$

 
8. (10 points) Fill out the following timing diagram for a rising-edge triggered JK flip-flop. Ignore all gate delays. $Q(0) = 1$.



 9. (10 points) Fill out the following timing diagram for a falling-edge triggered T flip-flop. Ignore all gate delays. $Q(0) = 1$.



 10. (10 points) Design a 3-bit counter that counts in the sequence given in the state diagram below. Use T flip-flops and a minimum number of external gates. Write each flip-flop equation, then draw the circuit diagram using the template below.





$$T_A = A'B' + C$$

$$T_B = B \oplus C$$

$$T_C = A(B + C')$$


A	B	C	A ⁺	B ⁺	C ⁺	T _A	T _B	T _C
0	0	0	1	0	0	1	0	0
0	0	1	X	X	X	X	X	X
0	1	1	1	1	1	1	0	0
0	1	0	0	0	0	0	1	0
1	0	0	1	0	1	0	0	1
1	0	1	0	1	1	1	1	0
1	1	1	0	1	0	1	0	1
1	1	0	X	X	X	X	X	X

 

 

11. (10 points) Design a 4-bit ripple counter that counts from 0–11. Use either D or T flip-flops (indicate which you choose) and a minimum number of external gates. Draw the circuit diagram using the template below. The flip-flop labeled A corresponds to the MSB of the counter, and the flip-flop labeled D corresponds to the LSB of the counter.

Flip-Flop Type: T

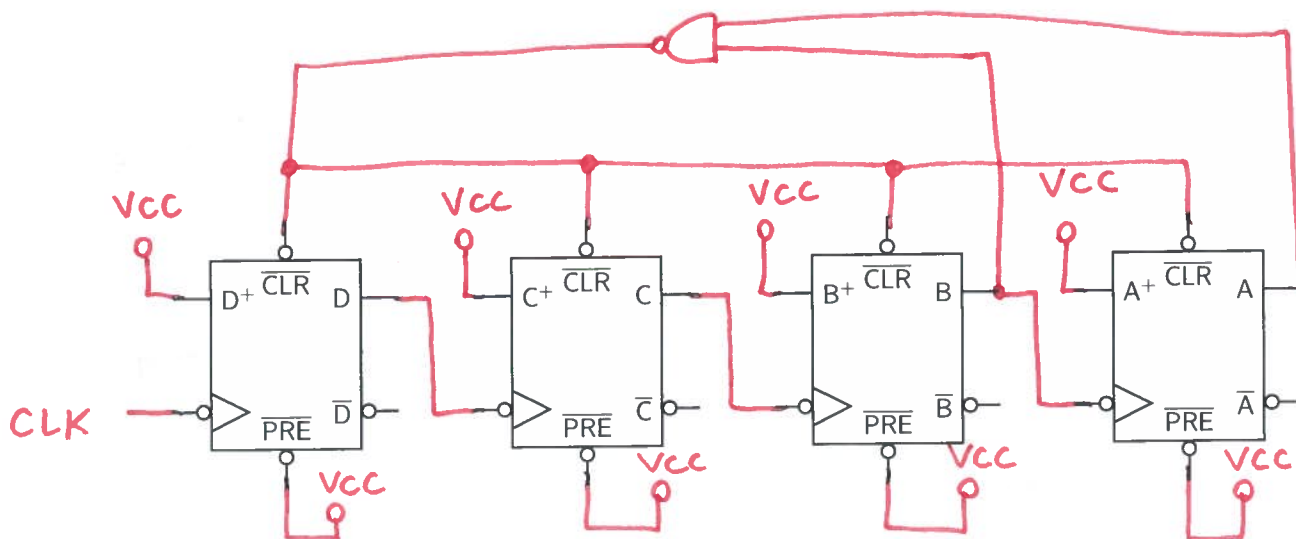


\overline{CLR} must go to zero when A & B are both 1. therefore

$$\overline{CLR} = \overline{AB}$$

11. (10 points) Design a 4-bit ripple counter that counts from 0–11. Use either D or T flip-flops (indicate which you choose) and a minimum number of external gates. Draw the circuit diagram using the template below. The flip-flop labeled A corresponds to the MSB of the counter, and the flip-flop labeled D corresponds to the LSB of the counter.

Flip-Flop Type: D

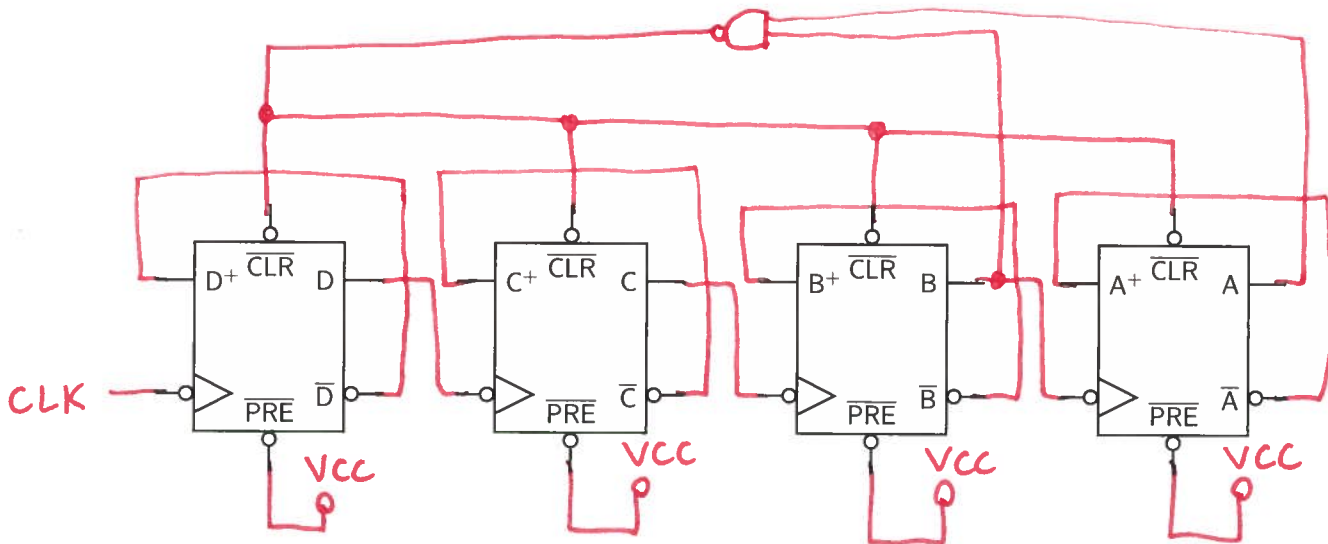

\overline{CLR} must go to zero when A & B are both 1. Therefore

$$\overline{C \cup R} = \overline{A \cap B}$$