
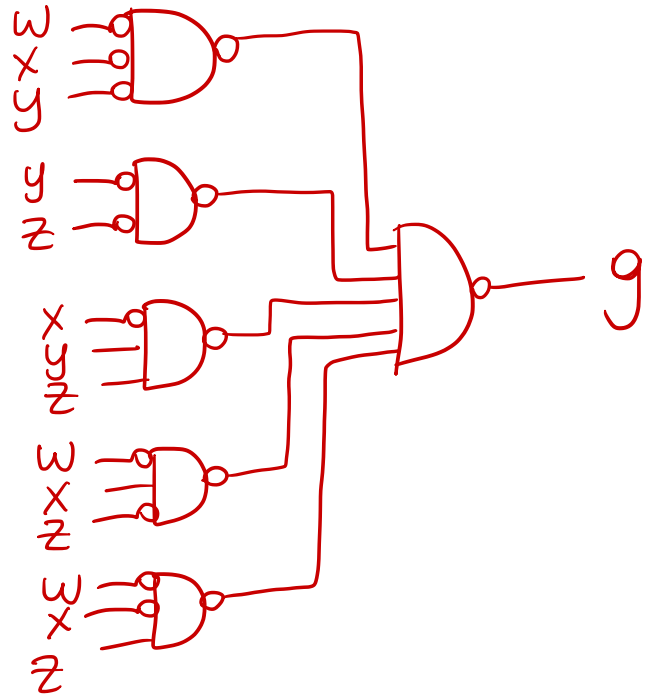


Name: SOLUTIONS

Read each question carefully before answering. Answer all parts. Show all work, calculations, and/or reasoning, otherwise no points will be awarded. Properly labeled loops **must be shown** on K-maps to receive credit. Assume that you have access to gates with as many inputs as you need. Point values are as indicated. Usage of XOR and XNOR gates is **not allowed** on this exam!

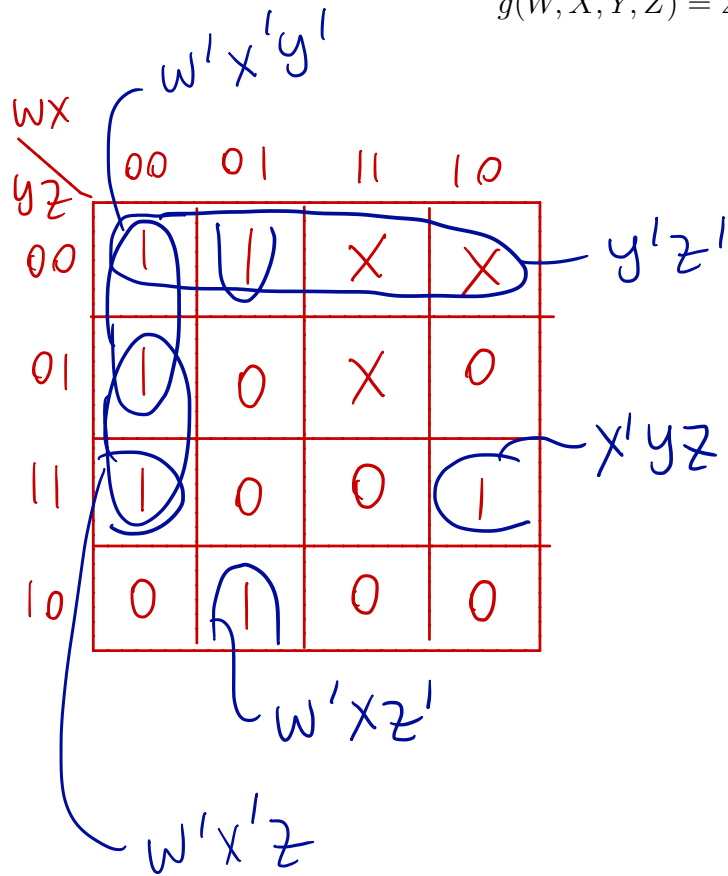1. (10 points) Draw the following as a hazard-free NAND-only circuit. **You may use bubbles on inputs, but not as output inverters!**

$$g(W, X, Y, Z) = \Sigma m(0, 1, 3, 4, 6, 11) + \Sigma d(8, 12, 13)$$



2. A sensor is capable of determining whether or not a car is speeding (driving faster than the speed limit) or driving dangerously (driving faster than 65 m.p.h. or driving more than 10 m.p.h. above the speed limit). The sensor receives the following codes. **AB** corresponds to the speed limit, and **CD** corresponds to the speed of the vehicle.

AB	Speed Limit	CD	Car's Speed
00	45 m.p.h.	00	≤ 45 m.p.h.
01	55 m.p.h.	01	46–55 m.p.h.
10	65 m.p.h.	10	56–65 m.p.h.
11	unused	11	> 65 m.p.h.

- (a) (10 points) Use a k-map to solve for F , which indicates if the car is speeding. All loops must be labeled to receive any credit.

		45	55	AB	65	
	CD	00	01	11	10	
≤ 45	00	0	0	X	0	
46–55	01	1	0	X	0	
> 65	11	1	1	X	1	CD
56–65	10	1	1	X	0	
		A'B'D		A'C		

$$F = A'B'D + A'C + CD$$

- (b) (10 points) Use a k-map to solve for G , which indicates if the car is driving dangerously. All loops must be labeled to receive any credit.

		45	55	AB	65
	CD	00	01	11	10
≤ 45	00	0	0	X	0
46-55	01	0	0	X	0
> 65	11	1	1	X	1
56-65	10	1	0	X	0

CD

$A'B'C$

G = $A'B'C + CD$

3. The following codes are used by a vending machine to determine the item being purchased (represented by the variables DE) and the number of money inserted into the machine (represented by the variables ABC). The machine has an output, V, which is 1 if enough money has been inserted to pay for the item.

ABC	Money Inserted	DE	Item & Cost
000	\$0.20	00	Snickers – \$0.70
001	\$0.30	01	Coke – \$0.60
010	\$0.40	10	Water – \$0.50
011	\$0.50	11	Chips – \$0.85
100	\$0.60		
101	\$0.70		
110	\$0.80		
111	\$0.90		

(a) (10 points) Find the minterms of V.

ABC		20¢	30¢	50¢	40¢	80¢	90¢	70¢	60¢	
DE		000	001	011	010	110	111	101	100	
00		0	0	0	0	1	1	1	0	70¢
01		0	0	0	0	1	1	1	1	60¢
11		0	0	0	0	0	1	0	0	85¢
10		0	0	1	0	1	1	1	1	50¢

$\Sigma m (14, 17, 18, 20, 21, 22, 24, 25, 26, 28, 29, 30, 31)$



THIS QUESTION CONTINUES ON THE NEXT PAGE

(b) (20 points) Use the Quine-McCluskey method to derive an equation for V.

	Column 1	Column 2	Column 3
TWO	17 10001 18 10010 20 10100 24 11000	17-21 10-01 17-25 1-001 18-22 10-10 18-26 1-010	17-21-25-29 1--01 18-22-26-30 1--10 20-21-28-29 1-10- 20-22-28-30 1-1-0 24-25-28-29 11-0- 24-26-28-30 11--0
THREE	14 01110 21 10101 22 10110 25 11001 26 11010 28 11100	20-21 1010- 20-22 101-0 20-28 1-100 24-25 1100- 24-26 110-0 24-28 11-00	28-29-30-31 111--
FOUR	29 11101 30 11110	14-30 -1110 21-29 1-101 22-30 1-110 25-29 11-01 26-30 11-10 28-29 1110- 28-30 111-0	
FIVE	31 11111	29-31 111-1 30-31 1111-	
PI's	BCDE' AD'E ADE' ACD' ACE' ABD' ABE' ABC		

V = $BCDE' + AD'E + ADE' + \begin{cases} ACD' + ABD' \\ ACE' + ABD' \\ ABE' + ACD' \\ ABE' + ACE' \end{cases}$

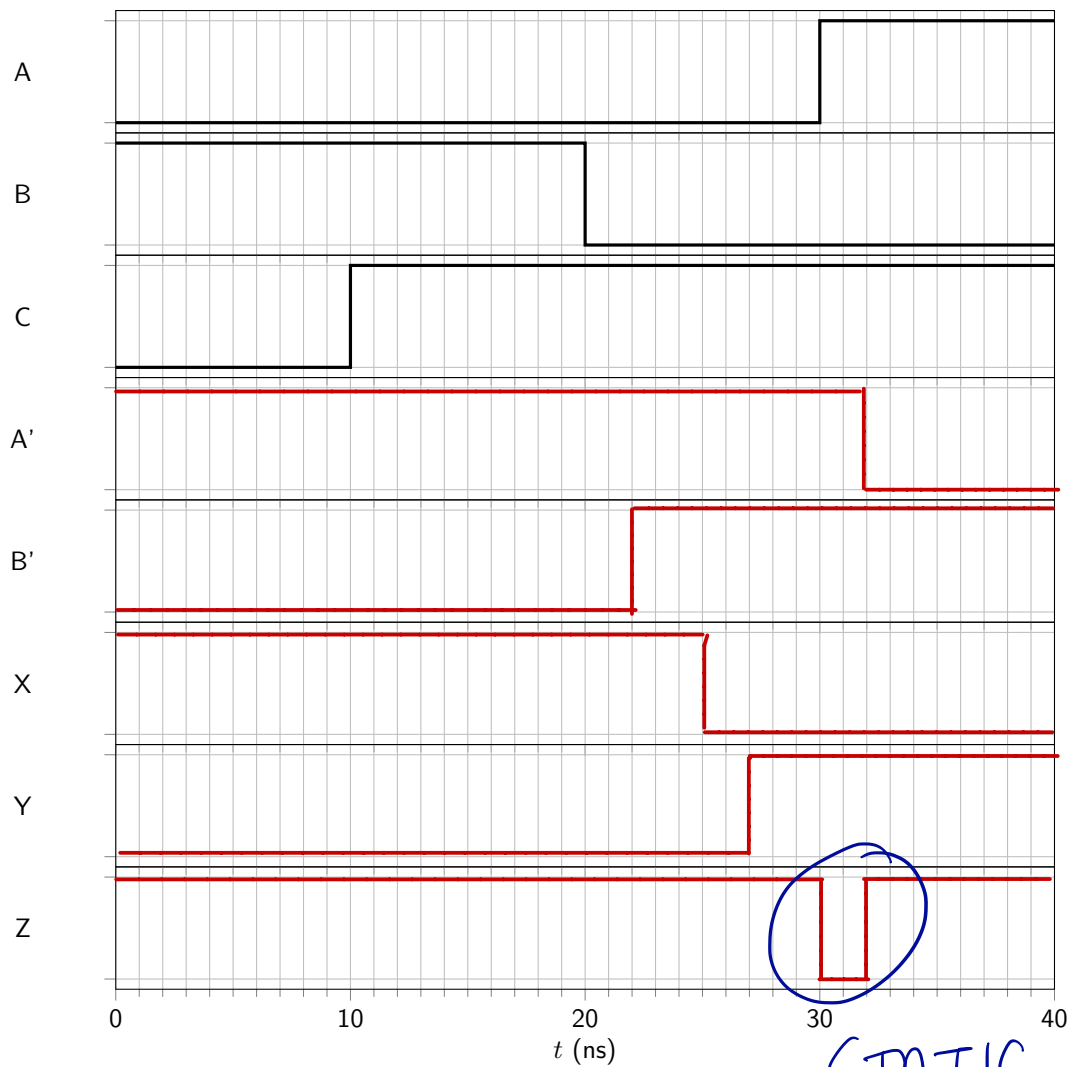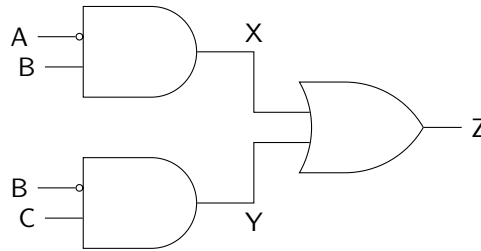4. (20 points) Draw a timing diagram for the following circuit, given gate delays of 2 ns for NOT gates, and 5 ns for AND and OR gates. Indicate any static hazards in the output signal



STATIC
ONE
HAZARD!

5. (25 points) Find the optimized implementation of the following two circuits. Show all work. How many gates and/or inputs do you save by implementing circuits together rather than individually?

$$X(A, B, C, D) = \Sigma m(2, 3, 4, 6, 7, 10, 12)$$

$$Y(A, B, C, D) = \Sigma m(4, 6, 7, 10, 12, 14, 15)$$

$BC'D$

X		AB			
CD		00	01	11	10
00	0	0	1	1	0
01	0	0	0	0	0
11	1	1	0	0	0
10	1	1	0	1	0

$A'C$

Y		AB			
CD		00	01	11	10
00	0	0	1	1	0
01	0	0	0	0	0
11	0	1	1	1	0
10	0	1	1	1	1

BC

$AB'CD'$

OPTIMIZED

$$X = A'C + BC'D + AB'CD'$$

$$Y = BC + BC'D + AB'CD'$$

SAVES 2 GATES
& 4 INPUTS