
 



Name: SOLUTIONS

Read each question carefully before answering. Answer all parts. Show all work, calculations, and/or reasoning, otherwise no points will be awarded. Properly labeled loops must be shown on K-maps. Point values are as indicated.

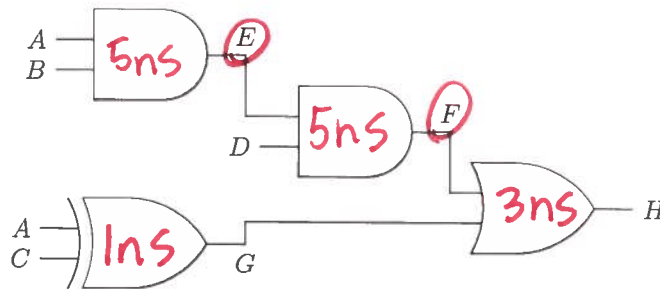1. (25 points) Given the following circuit diagram, fill out the timing diagram for E , F , G and H given the values of inputs A , B , C , and D . Indicate any hazards, given that H should be logic HIGH the entire duration of this timing diagram. Each XOR gate has a delay of 1 ns, each AND gate has a delay of 5 ns, and each OR gate has a delay of 3 ns.



 
2. Your buddy (who may or may not be any good at digital systems), shows you the following diagram of a circuit they wired up.



(a) (5 points) What is the MUX equation corresponding to the above circuit?


$$F = \underline{B'C'(A'+D')} + \underline{B'C(A+D')} + \underline{BC'(A'D')} + \underline{BC(A'D)}$$

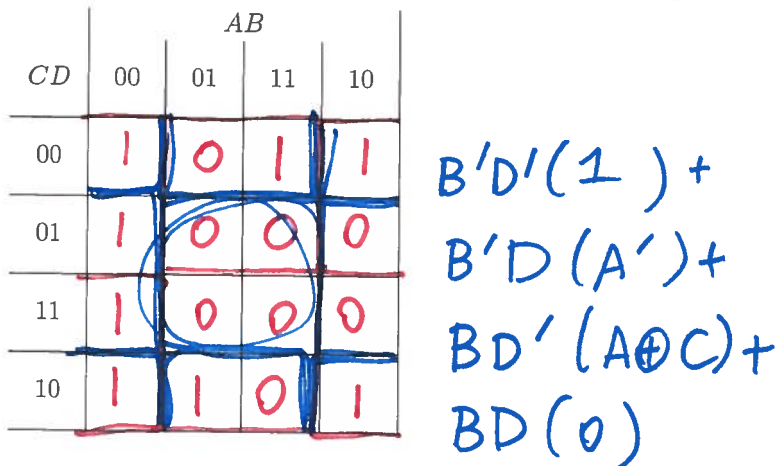(b) (5 points) Fill out the following K-map based on the above equation.




(c) (10 points) Find a MUX implementation of this circuit that requires a minimum number of gates. Write the MUX equation and fill out the corresponding circuit diagram.


F = _____

 

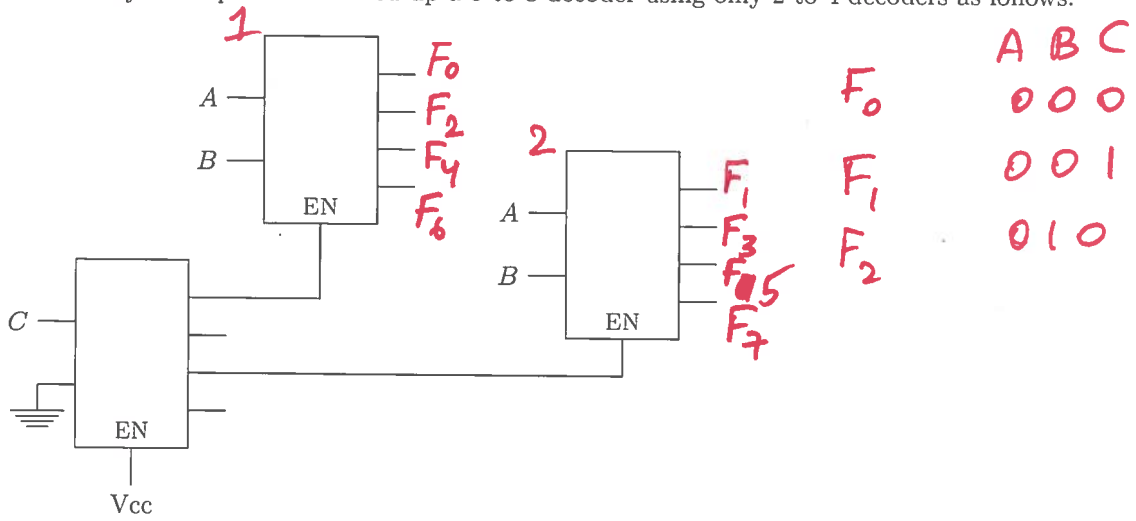
3. Your buddy from question 2 wired up a 3 to 8 decoder using only 2 to 4 decoders as follows.



 - (a) (7 points) Label the above circuit diagram with outputs from $F_0 - F_7$.
- (b) (3 points) Using only the decoder outputs, and a minimum number of 2-input gates, use the above schematic to draw a circuit diagram to implement the following function:



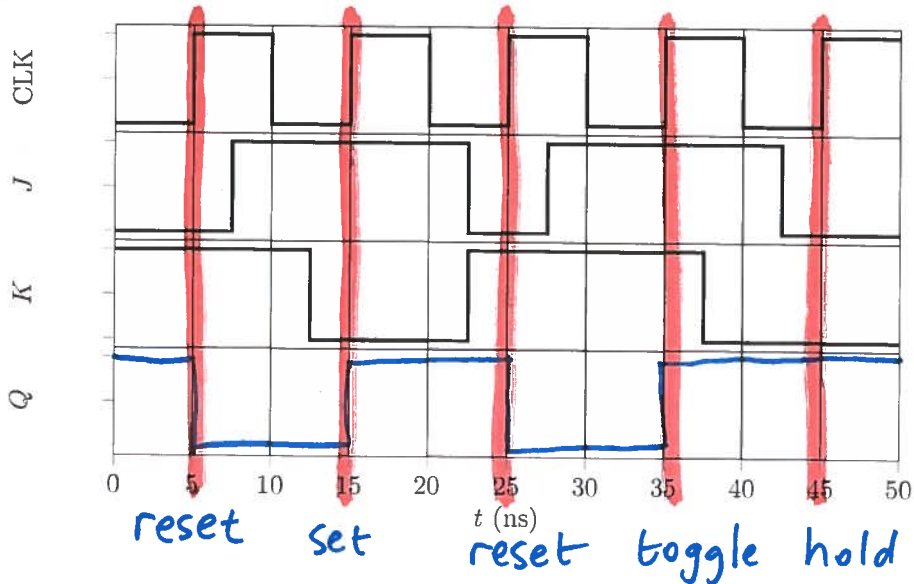4. (10 points) Fill out the following timing diagram for a rising-edge triggered JK flip-flop. Ignore propagation delays. The value of Q is initially equal to 1.



~~0~~
~~1~~
~~2~~
~~3~~
~~4~~
~~5~~
~~6~~
~~7~~

5. (30 points) Design a 3-bit counter that counts in the sequence (001, 101, 010, 110, 000, 011...) using T flip-flops and a minimum number of external gates. Determine the logic required on the input of each flip-flop, then draw the circuit diagram using the template below.

1 5 2 6 0 3

A	B	C	A ⁺	B ⁺	C ⁺	T _A	T _B	T _C
0	0	0	0	1	1	0	1	1
0	0	1	1	0	1	1	0	0
0	1	0	1	1	0	1	0	0
0	1	1	0	0	1	0	1	0
1	0	0	X	X	X	X	X	X
1	0	1	0	1	0	1	1	1
1	1	0	0	0	0	1	1	0
1	1	1	X	X	X	X	X	X

