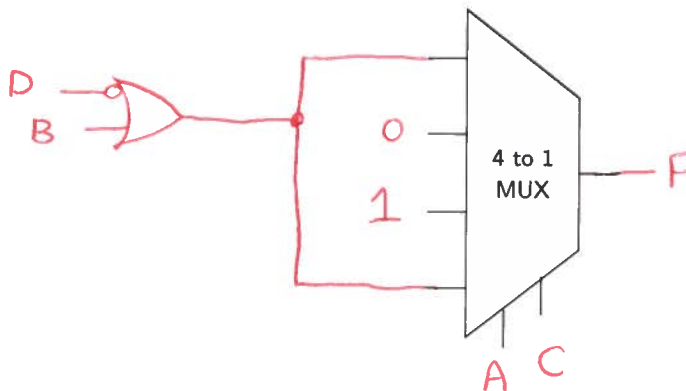


Name: SOLUTIONS

Read each question carefully before answering. Answer all parts. Show all work, calculations, and/or reasoning, otherwise no points will be awarded. Properly labeled loops must be shown on K-maps. Point values are as indicated.


1. (20 points) You receive two 2-bit numbers designated as  $AB$  and  $CD$ . If  $AB \geq CD$ , an LED should turn on. The output of this function,  $F$ , will therefore be 1 if the LED should be on. Otherwise  $F$  will be 0. Implement this using a 4 to 1 MUX and a minimum number of external gates. Fill in the corresponding circuit diagram. Clearly indicate your control bits, and include your multiplexer equation at the bottom of the page.

		0	1	AB	3	2
	CD	00	01	11	10	
0	00	1	1	1	1	
1	01	0	1	1	1	
3	11	0	0	1	0	
2	10	0	0	1	1	




$$F = A'C'(D'+B) + A'C(0) + AC'(1) + AC(D'+B)$$

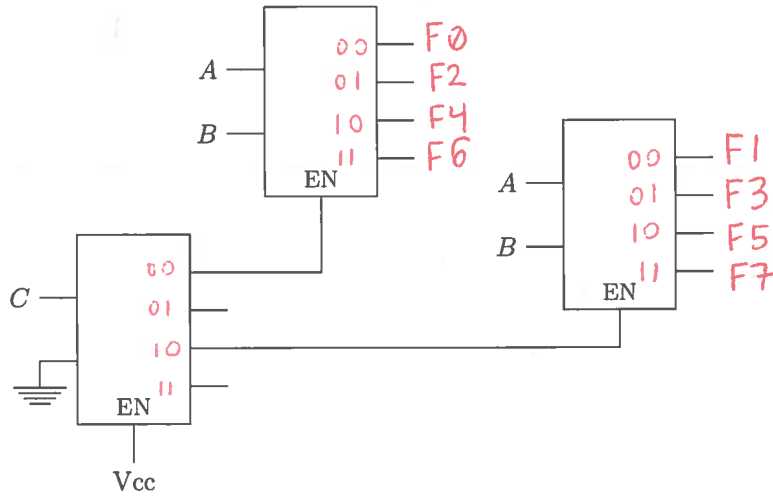2. (20 points) Your buddy wired up a 3 to 8 decoder using only 2 to 4 decoders as follows. The MSB of the control bits is  $A$ , and the LSB of the control bits is  $C$ . Label the circuit diagram with the correct outputs from  $F_0 - F_7$ .



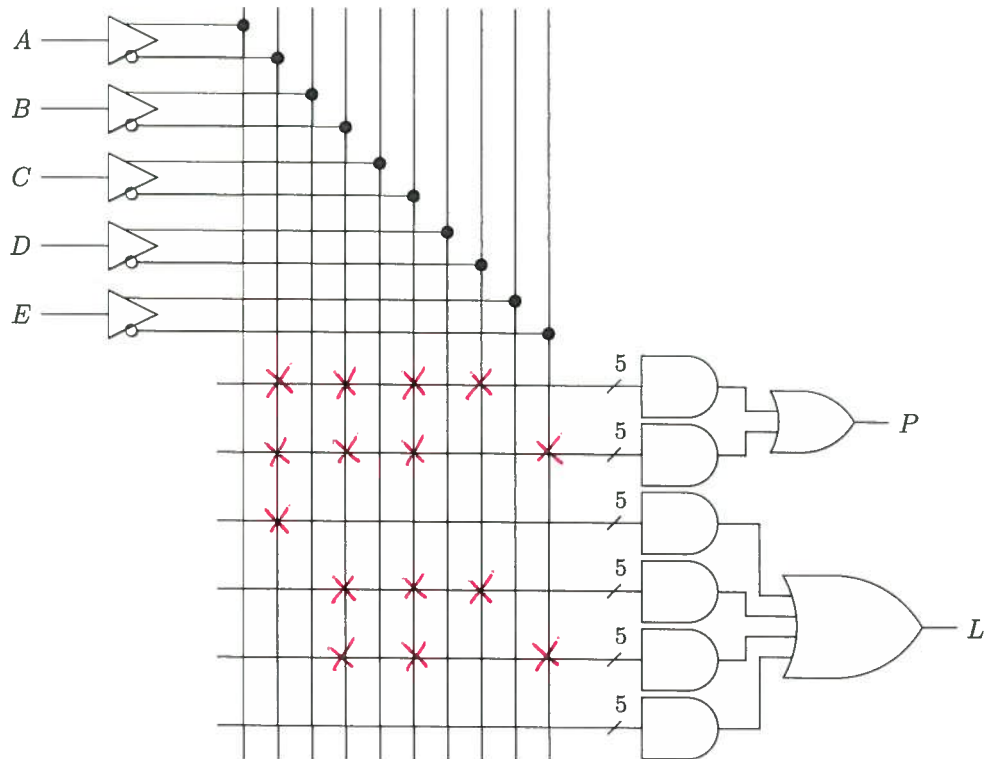
3. (25 points) A sensor on a car tire sends a 5-bit binary signal ( $ABCDE$ ) that represents the tire pressure in PSI. The output  $L$  (low pressure) should be 1 if the pressure is less than 19. The output  $P$  (puncture) should be 1 if the pressure is less than 3. Use the following PAL diagram to implement outputs  $L$  and  $P$ . You will **not** need to add any gates to the PAL diagram!




$$P = A'B'C'D' + A'B'C'E'$$

$$L = A' + B'C'D' + B'C'E'$$

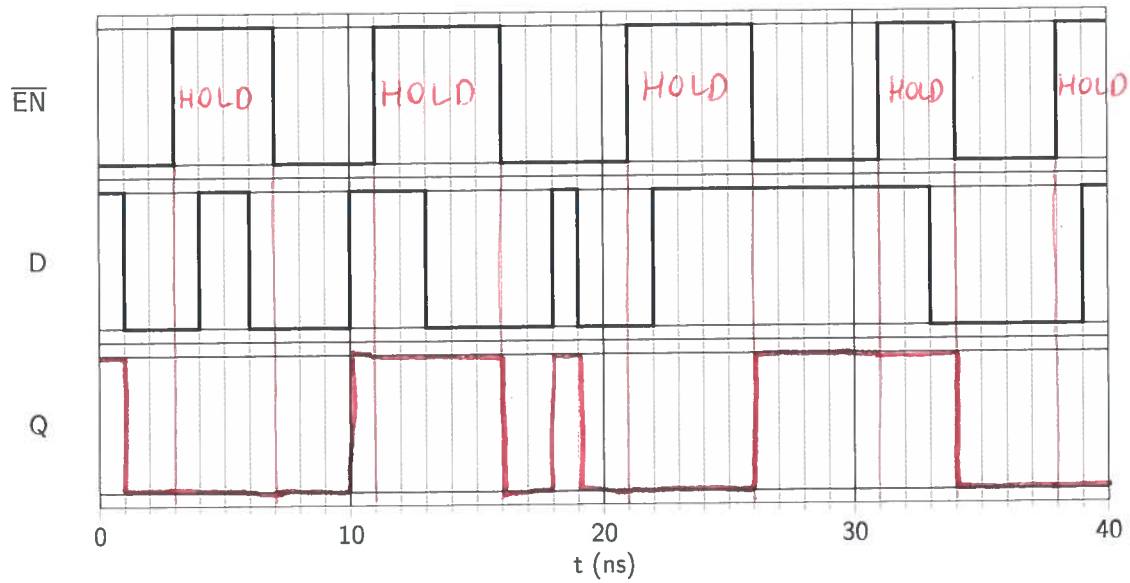
4. (10 points) Fill out the following timing diagram for an active-low gated D latch. Ignore all gate delays.  $Q(0) = 0$ .



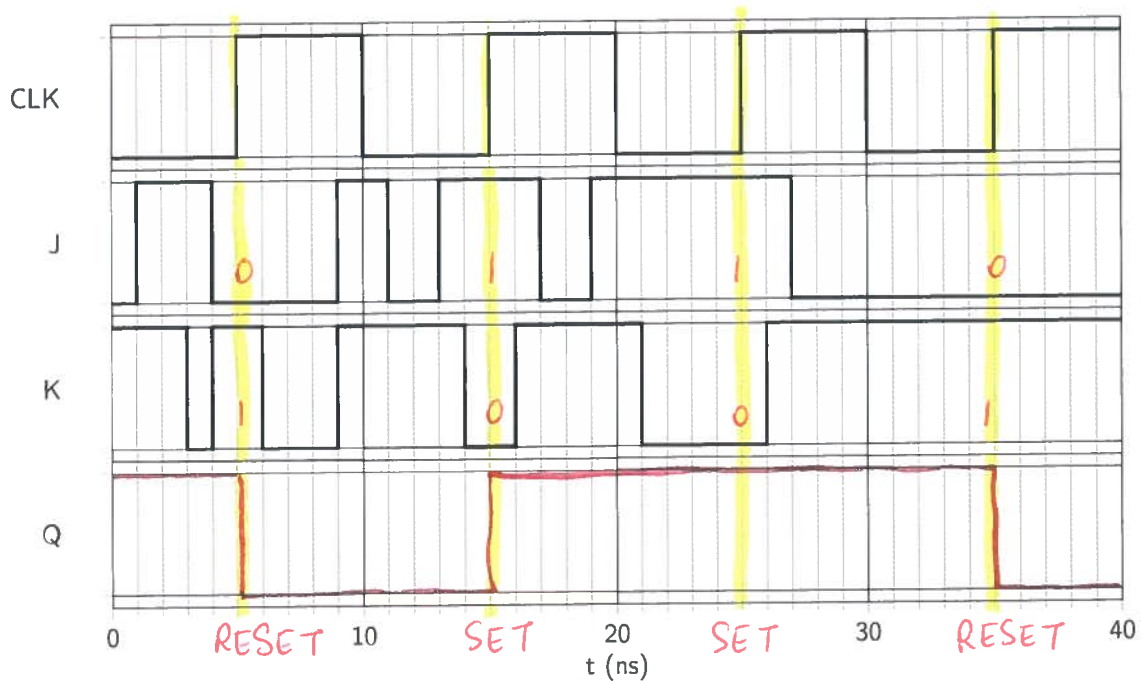5. (10 points) Fill out the following timing diagram for a rising-edge triggered JK flip-flop. Ignore all gate delays.  $Q(0) = 1$ .



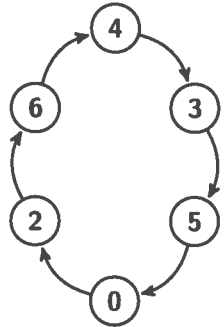6. (25 points) Design a 3-bit counter that counts in the sequence given in the state diagram below. Use T flip-flops and a minimum number of external gates. Write each flip-flop equation, then draw the circuit diagram using the template below.



$T_A = A \oplus B$

$T_B = B' \oplus C + AB$

$T_C = AB'$

	A	B	C	A <sup>+</sup>	B <sup>+</sup>	C <sup>+</sup>	T <sub>A</sub>	T <sub>B</sub>	T <sub>C</sub>
0	0	0	0	0	1	0	0	1	0
1	0	0	1	X	X	X	X	X	X
3	0	1	1	1	0	1	1	1	0
2	0	1	0	1	1	0	1	0	0
4	1	0	0	0	1	1	1	1	1
5	1	0	1	0	0	0	1	0	1
7	1	1	1	X	X	X	X	X	X
6	1	1	0	1	0	0	0	1	0

