

Name: \_\_\_\_\_

**SOLUTIONS**

Read each question carefully before answering. Answer all parts. Show all work, calculations, and/or reasoning, otherwise no points will be awarded. Properly labeled loops must be shown on K-maps. Point values are as indicated.

1. Your buddy (who may or may not be any good at digital systems) gives you the following state table...

Current State	Next State		Output	
	X = 0	X = 1	X = 0	X = 1
A	F	B	0	0
B	E	A	0	1
C	H	G	0	1
D	H	D	1	0
E	B	F	1	1
F	G	B	0	0
G	A	C	0	0
H	C	A	1	1

- (a) (5 points) Is this a Mealy machine or a Moore machine? Explain how you know.


**MEALY - The output depends on the input value!**

- (b) (10 points) Use an implication table to reduce the number of states. Indicate which (if any) states are equivalent.

$$A \equiv F \equiv G$$

$$B \equiv C$$


$$E \equiv H$$

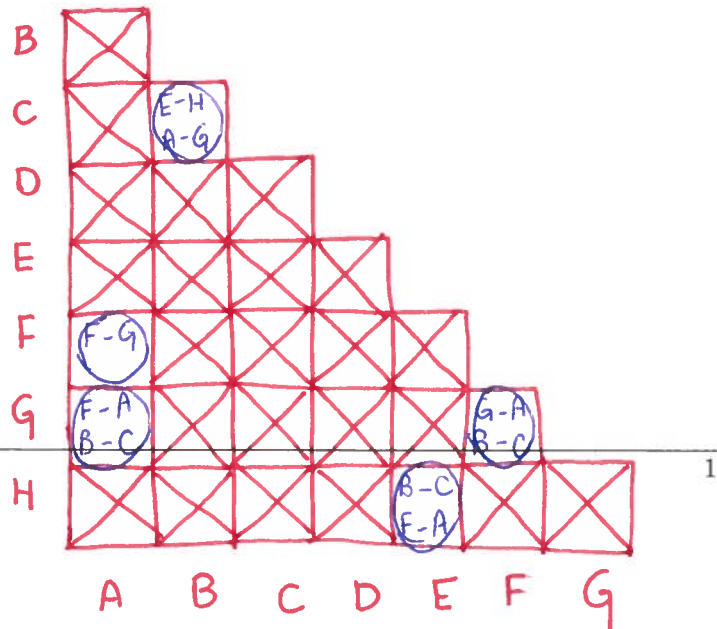

(c) (10 points) Fill out a new (reduced) state table.

Current State	Next State		Output	
	X = 0	X = 1	X = 0	X = 1
A	A	B	0	0
B	E	A	0	1
D	E	D	1	0
E	B	A	1	1

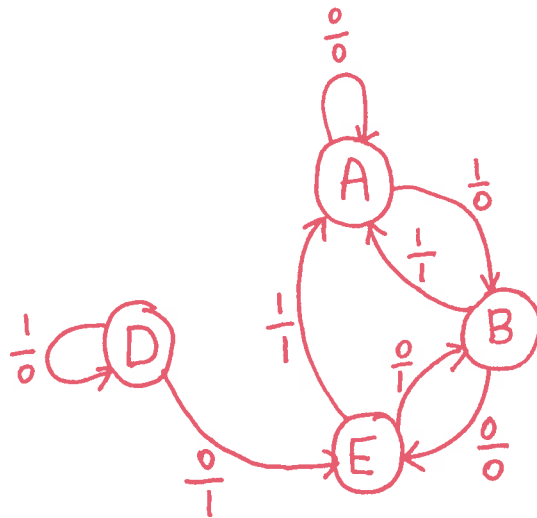(d) (10 points) Draw a reduced state diagram.



2. You wish to design a Moore machine non-overlapping sliding window detector that has an output  $Z = 1$  when the input sequence contains **101101**.

(a) (10 points) Clearly define all states that are required to implement this circuit.

$S_0$ : reset  $z = 0$

$S_1 = 1, 11, 111 \dots z = 0$

$S_2 = 10 z = 0$


$S_3 = 101 z = 0$

$S_4 = 1011 z = 0$


$S_5 = 10110 z = 0$

$S_6 = 101101 z = 1$

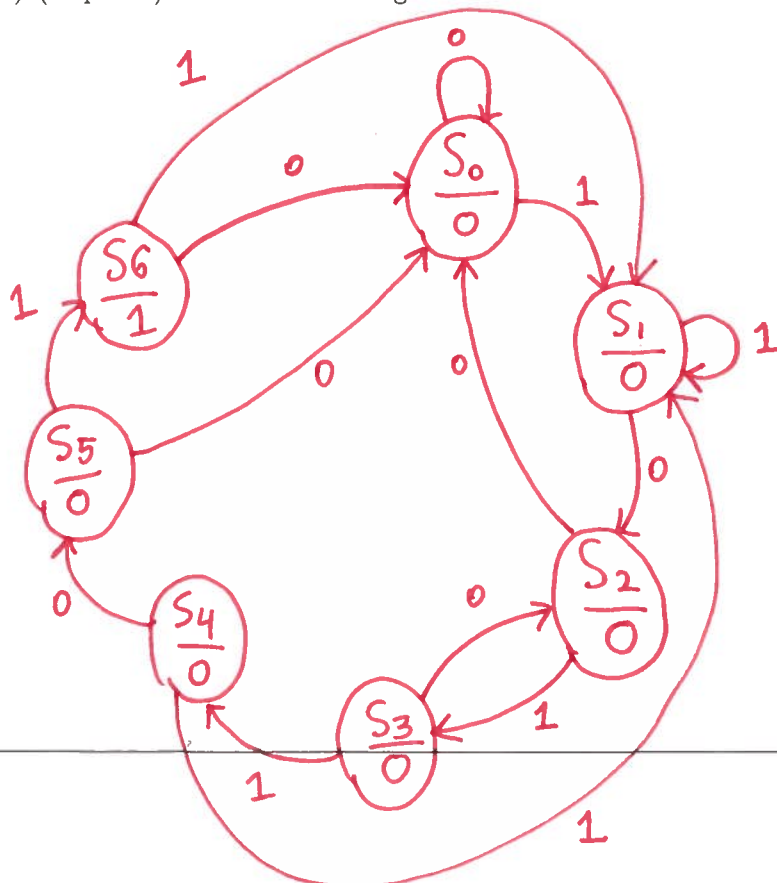(b) (10 points) Draw the state diagram for this circuit.



3. Given the following state diagram...

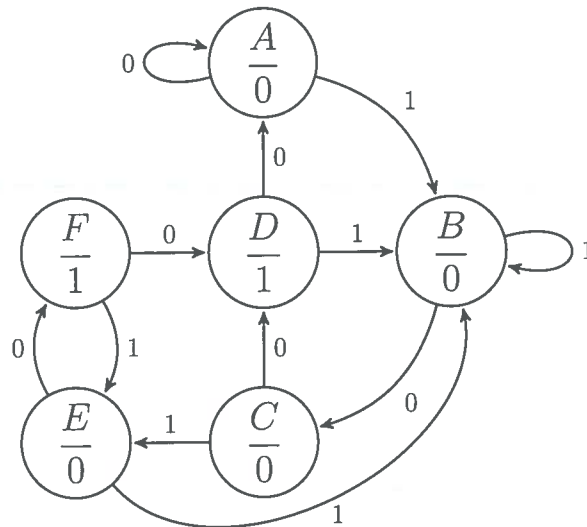

(a) (10 points) ...fill the corresponding state table.

Current State	Next State		Output
	$X = 0$	$X = 1$	
A	A	B	0
B	C	B	0
C	D	E	0
D	A	B	1
E	F	B	0
F	D	E	1

(b) (5 points) There are no redundant states! (Although, feel free to create an implication table and check if you don't believe me.) How many flip-flops will you need to implement this circuit?

3 flip-flops

(c) (10 points) Implement the guidelines for state assignment.

Guideline 1:

- A, D
- C, F x 2
- A, B, D, E

Guideline 2:

- A, B x 2      • F, B
- C, B
- D, E x 2

Guideline 3:

- D, F
- A, B, C, E

(d) (5 points) Use a K-map to determine state assignments for each state. Indicate the binary values for each state.

	A	
BC	0	1
00	B	E
01	A	D
11	C	F
10	X	X

A = 001  
 B = 000  
 C = 011  
 D = 101  
 E = 100  
 F = 111

(e) (10 points) Fill out the corresponding transition table.

Current State	Next State						Output (Z)
	X = 0			X = 1			
<b>B</b> 000	0	1	1	0	0	0	0
<b>A</b> 001	0	0	1	0	0	0	0
<b>C</b> 011	1	0	1	1	0	0	0
010	X	X	X	X	X	X	X
<b>E</b> 100	1	1	1	0	0	0	0
<b>D</b> 101	0	0	1	0	0	0	1
<b>F</b> 111	1	0	1	1	0	0	1
110	X	X	X	X	X	X	X

(f) (5 points) Derive an equation for Z.

BC	A	
	0	1
00	0	0
01	0	1
11	0	1
10	X	X

AC

$Z = AC$

(g) (10 points) Using  $D$  flip-flops, derive an equation for each flip-flop.

	XA			
BC	00	01	11	10
00	0	1	0	0
01	0	0	0	0
11	1	1	1	1
10	X	X	X	X

→ B

→  $X'AC'$

$$A^+ = B + X'AC'$$

	XA			
BC	00	01	11	10
00	1	1	0	0
01	0	0	0	0
11	0	0	0	0
10	X	X	X	X

→  $X'C'$

$$B^+ = X'C'$$

	XA			
BC	00	01	11	10
00	1	1	0	0
01	1	1	0	0
11	1	1	0	0
10	X	X	X	X

→  $X'$

$$C^+ = X'$$