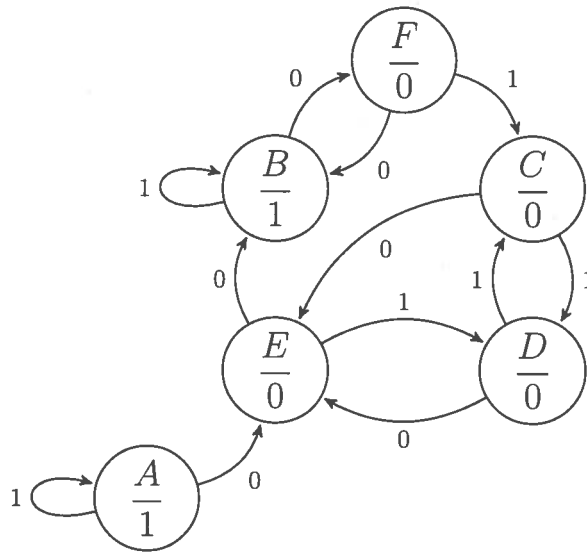


Name: SOLUTIONS

Read each question carefully before answering. Answer all parts. Show all work, calculations, and/or reasoning, otherwise no points will be awarded. Properly labeled loops must be shown on K-maps. Point values are as indicated.


1. Your buddy (who may or may not be any good at digital systems) shows you the following state diagram...



- (a) (10 points) Fill out the corresponding state table.

Current State	Next State		Output
	X = 0	X = 1	
A	E	A	1
B	F	B	1
C	E	D	0
D	E	C	0
E	B	D	0
F	B	C	0

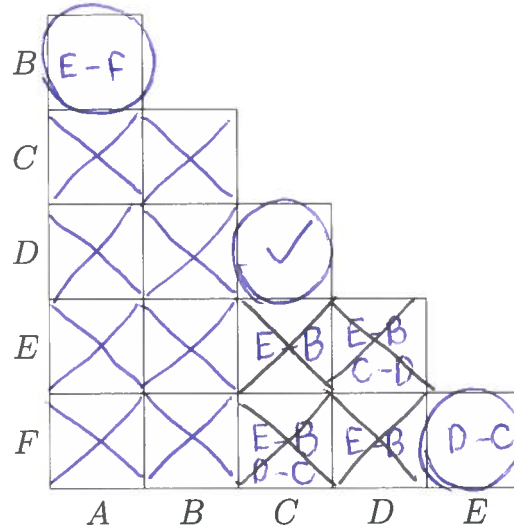(b) (10 points) Use an implication table to reduce the number of states. Indicate which (if any) states are equivalent.




(c) (10 points) Fill out a new state table.

Current State	Next State		Output
	$X = 0$	$X = 1$	
A	E	A	1
C	E	C	0
E	A	C	0


- (d) (10 points) Create state assignments for the states (indicate what they are) and fill out the corresponding transition table.

Current State		Next State		Output
		$X = 0$	$X = 1$	
A	00	10	00	1
C	01	10	01	0
	11	XX	XX	X
E	10	00	01	0

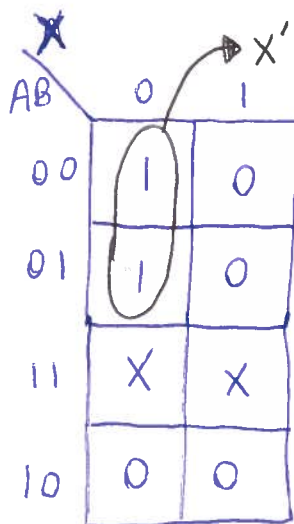
- (e) (10 points) Use K-maps, Boolean algebra or Quine-McCluskey to derive next-state equations for each flip-flop, as well as an equation for the output, Z .



$$A^+ = X'A'$$

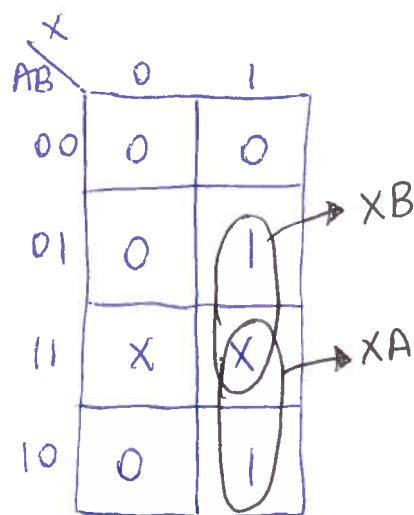


$$B^+ = X(A+B)$$

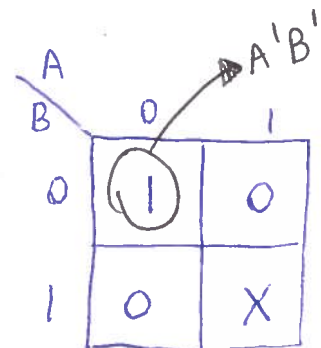

$$Z = A'B'$$

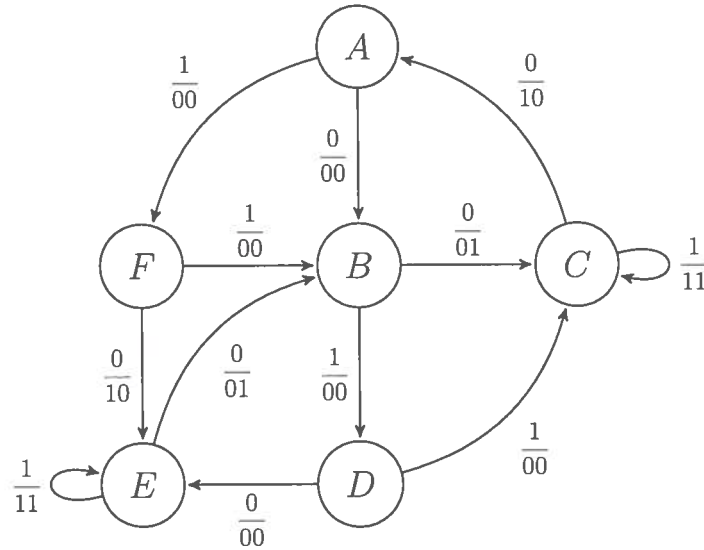2. The following is a fully reduced state diagram and state table for a Mealy machine with two outputs, Y and Z .



Current State	Next State		Outputs (YZ)	
	$X = 0$	$X = 1$	$X = 0$	$X = 1$
010 <i>A</i>	<i>B</i>	<i>F</i>	00	00
111 <i>B</i>	<i>C</i>	<i>D</i>	01	00
011 <i>C</i>	<i>A</i>	<i>C</i>	10	11
001 <i>D</i>	<i>E</i>	<i>C</i>	00	00
110 <i>E</i>	<i>B</i>	<i>E</i>	01	11
101 <i>F</i>	<i>E</i>	<i>B</i>	10	00

- (a) (10 points) Use the guidelines for state assignment to find reduced binary representations for each state.

Guideline 1:

AE ✓
DF ✓
CD ✓

Guideline 2:

BF ✓
CD ✓
AC ✓
EC
BE x 2 ✓

Guideline 3:

AD ABDF
BE ✓ CE
CF

- (b) (10 points) Use a K-map to determine state assignments for each state. Indicate the binary values for each state.

BC	A	
	0	1
00	X	X
01	D	F
11	C	B
10	A	E

A = 010
B = 111
C = 011
D = 001
E = 110
F = 101

(c) (10 points) Fill out the corresponding transition table.

Current State	Next State		Outputs (YZ)	
	X = 0	X = 1	X = 0	X = 1
000	XXX	XXX	XX	XX
D 001	110	011	00	00
C 011	010	011	10	11
A 010	111	101	00	00
100	XXX	XXX	XX	XX
F 101	110	111	10	00
B 111	011	001	01	00
E 110	111	110	01	11

(d) (10 points) Derive an equation for each output variable.

y

BC	XA			
	00	01	11	10
00	X	X	X	X
01	0	1	0	0
11	1	0	0	1
10	0	0	1	0

$A'BC$ (points to 11,00)
 $X'AB'$ (points to 00,01)
 XAC' (points to 10,11)

z

BC	XA			
	00	01	11	10
00	X	X	X	X
01	0	0	0	0
11	0	1	0	1
10	0	1	1	0

$XA'BC$ (points to 11,11)
 $X'AB$ (points to 10,01)
 ABC' (points to 10,11)

$$y = A'BC + A(X'B' + XC')$$

$$z = AB(X' + C') + XA'BC$$

(e) (20 points) Using D flip-flops, derive an equation for each flip-flop.

A^+

	XA			
BC	00	01	11	10
00	X	X	X	X
01	1	1	1	0
11	0	0	0	0
10	1	1	1	1

Annotations: $X'B'$ (pointing to 00, 01), AB' (pointing to 11, 10), C' (pointing to 10 row)

$$A^+ = C' + B'(X' + A)$$

B^+

	XA			
BC	00	01	11	10
00	X	X	X	X
01	1	1	1	1
11	1	1	0	1
10	1	1	1	0

Annotations: B' (pointing to 01, 11), $A'C$ (pointing to 11, 10), X' (pointing to 00, 01), AC' (pointing to 10, 11)

$$B^+ = X' + B' + A \oplus C$$

C^+

	XA			
BC	00	01	11	10
00	X	X	X	X
01	0	0	1	1
11	0	1	1	1
10	1	1	0	1

Annotations: XC (pointing to 01, 11), $A'C'$ (pointing to 10, 11), $X'AB$ (pointing to 01, 10), $No!$ (pointing to 00, 10)

$$C^+ = XC + A'C' + X'AB$$