

Name: SOLUTIONS

Read each question carefully before answering. Answer all parts. Show all work, calculations, and/or reasoning, otherwise no points will be awarded. Properly labeled loops must be shown on K-maps. Point values are as indicated.

1. (25 points) Design a Mealy Machine that generates an even parity bit ( $Z$ ) for the 3 preceding bits of input ( $X$ ). An example sequence of inputs and outputs are given below. Define all of the states and derive a reduced state table. (There are exactly enough rows on the state table template that is given below.)

$X =$	0	0	1	1	0	1	1	0	0	1	0	1	0	1	0	0	1	1	1	1
$Z =$	0	0	1	0	0	0	0	0	1	1	1	0	1	0	1	1	1	0	1	1

 $S_0$  reset

A 0

B 1

C 00

D 01

E 10

F 11

Current State	Next State		Output	
	$X = 0$	$X = 1$	$X = 0$	$X = 1$
$S_0$	A	B	0	0
A	C	D	0	0
B	E	F	0	0
C	C	D	0	1
D	E	F	1	0
E	C	D	1	0
F	E	F	0	1

2. Your buddy (who may or may not be any good at digital systems) gives you the following state table...

Current State	Next State		Output	
	X = 0	X = 1	X = 0	X = 1
A	F	B	0	0
B	E	A	0	1
C	H	G	0	1
D	H	D	1	0
E	B	F	1	1
F	G	B	0	0
G	A	C	0	0
H	C	A	1	1

- (a) (5 points) Is this a Mealy machine or a Moore machine? Explain how you know.

MEALY - OUTPUTS DEPEND ON INPUT  
& CURRENT STATE

- (b) (10 points) Use an implication table to reduce the number of states. Indicate which (if any) states are equivalent.

B	X						
C	X	E-H A-G					
D	X	X	X				
E	X	X	X	X			
F	F-G	X	X	X	X		
G	F-A B-C	X	X	X	X	A-A B-C	
H	X	X	X	X	B-G F-A	X	X
	A	B	C	D	E	F	G

$A \equiv F \equiv G$   
 $B \equiv C$   
 $E \equiv H$

2

3. (20 points) Determine if the two sequential circuits (given below as state tables) are equivalent. Justify your answer.

C.S.	N.S.		YZ	C.S.	N.S.		YZ
	X = 0	X = 1			X = 0	X = 1	
A	B	D	00	S <sub>0</sub>	S <sub>2</sub>	S <sub>4</sub>	00
B	D	B	01	S <sub>1</sub>	S <sub>1</sub>	S <sub>2</sub>	11
C	C	B	11	S <sub>2</sub>	S <sub>4</sub>	S <sub>5</sub>	01
D	A	C	10	S <sub>3</sub>	S <sub>5</sub>	S <sub>4</sub>	00
				S <sub>4</sub>	S <sub>3</sub>	S <sub>1</sub>	10
				S <sub>5</sub>	S <sub>4</sub>	S <sub>2</sub>	01

	S <sub>0</sub>	S <sub>1</sub>	S <sub>2</sub>	S <sub>3</sub>	S <sub>4</sub>	S <sub>5</sub>
A	B-S <sub>2</sub> D-S <sub>4</sub>	X	X	B-S <sub>5</sub> D-S <sub>4</sub>	X	X
B	X	X	D-S <sub>4</sub> B-S <sub>5</sub>	X	X	D-S <sub>4</sub> B-S <sub>2</sub>
C	X	C-S <sub>1</sub> ✓ B-S <sub>2</sub>	X	X	X	X
D	X	X	X	X	A-S <sub>3</sub> C-S <sub>1</sub>	X

THEY ARE EQUIVALENT

$$A \equiv S_0 \equiv S_3$$


$$B \equiv S_2 \equiv S_5$$

$$C \equiv S_1$$

$$D \equiv S_4$$

4. (25 points) You wish to design a Moore machine non-overlapping sliding window detector that has an output  $Z = 1$  when the input sequence contains 10101. Clearly define all states that are required to implement this circuit, then draw the state diagram for this circuit.

$S_0$	reset, 0, 00...	$Z=0$
$S_1$	1, 11...	$Z=0$
$S_2$	10	$Z=0$
$S_3$	101	$Z=0$
$S_4$	1010	$Z=0$
$S_5$	10101	$Z=1$

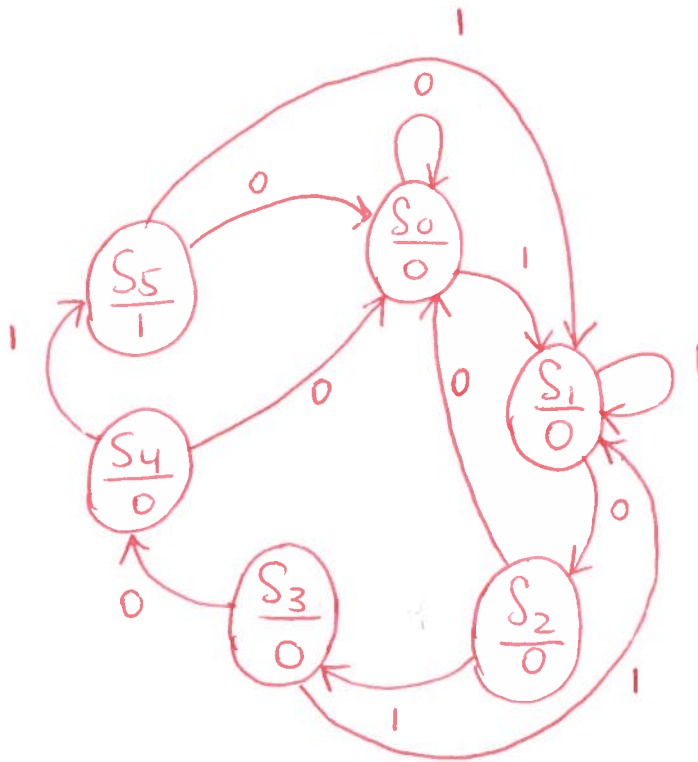

5. The following is a fully reduced state table.

Current State	Next State		Output
	$X = 0$	$X = 1$	
$A$	$A$	$B$	0
$B$	$C$	$B$	0
$C$	$D$	$E$	0
$D$	$A$	$B$	1
$E$	$F$	$B$	0
$F$	$D$	$E$	1

(a) (5 points) How many flip-flops will you need to implement this circuit?

3 FLIP-FLOPS

(b) (5 points) Implement the guidelines for state assignment.

Guideline 1:

$AD$  ✓  
 $CF \times 2$  ✓  
 $ABDE$

Guideline 2:

$AB \times 2$  ✓  
 $CB$  ✓  
 $DE \times 2$  ✓  
 $FB$

Guideline 3:

$ABCE$   
 $DF$

(c) (5 points) Use a K-map to determine state assignments for each state. Indicate the binary values for each state.

$C$	$AB$			
	00	01	11	10
0	$C$	$B$	$E$	$\times$
1	$F$	$A$	$D$	$\times$

$A = 011$   
 $B = 010$   
 $C = 000$   
 $D = 111$   
 $E = 110$

(d) (10 points) Fill out the corresponding transition table.

Current State		Next State						Output (Z)
		X = 0			X = 1			
C	000	1	1	1	1	1	0	0
F	001	1	1	1	1	1	0	1
A	011	0	1	1	0	1	0	0
B	010	0	0	0	0	1	0	0
	100	X	X	X	X	X	X	X
	101	X	X	X	X	X	X	X
D	111	0	1	1	0	1	0	1
E	110	0	0	1	0	1	0	0